

Brian Hert  
11-3-2023

HW#5  
CSc 137

Problem I: Consider the sequential circuit in Figure 5.31 where the adder is a CLA. Its simplified circuit is shown in Figure 5.32. Assuming that the Flip-Flops register set-up time, clock-to-q, and clock-skew are each 0.1 ns, AND gate = 0.2 ns and EXOR = 0.3 ns determine the upper bound for its clock frequency. (10 pts)

1)

Longest Path Delay

$$= \Delta_{AND} + \Delta_{EXOR} + \Delta_{AND} + \Delta_{TO_{Flip}}$$

$$= 0.2ns + 0.3ns + 0.2ns + 0.3ns$$

$$= 1.0ns$$

Upper Bound Frequency

For the first flip flop from right in figure 5.32 the clock-skew time will be  $(0.1+0.1)=0.2ns$ .

Now adding the clock-to-Q time and register


Setting up time to this we get, 0.4 ns. So the

clock frequency maximum should be  $1/(0.4ns) = 2.5 * 10^9 Hz$

$$1/(0.4ns) = 2.5 * 10^9 Hz$$

1

3)

 

Problem III: Textbook problem 5.11 (only FSD) (5 pts)